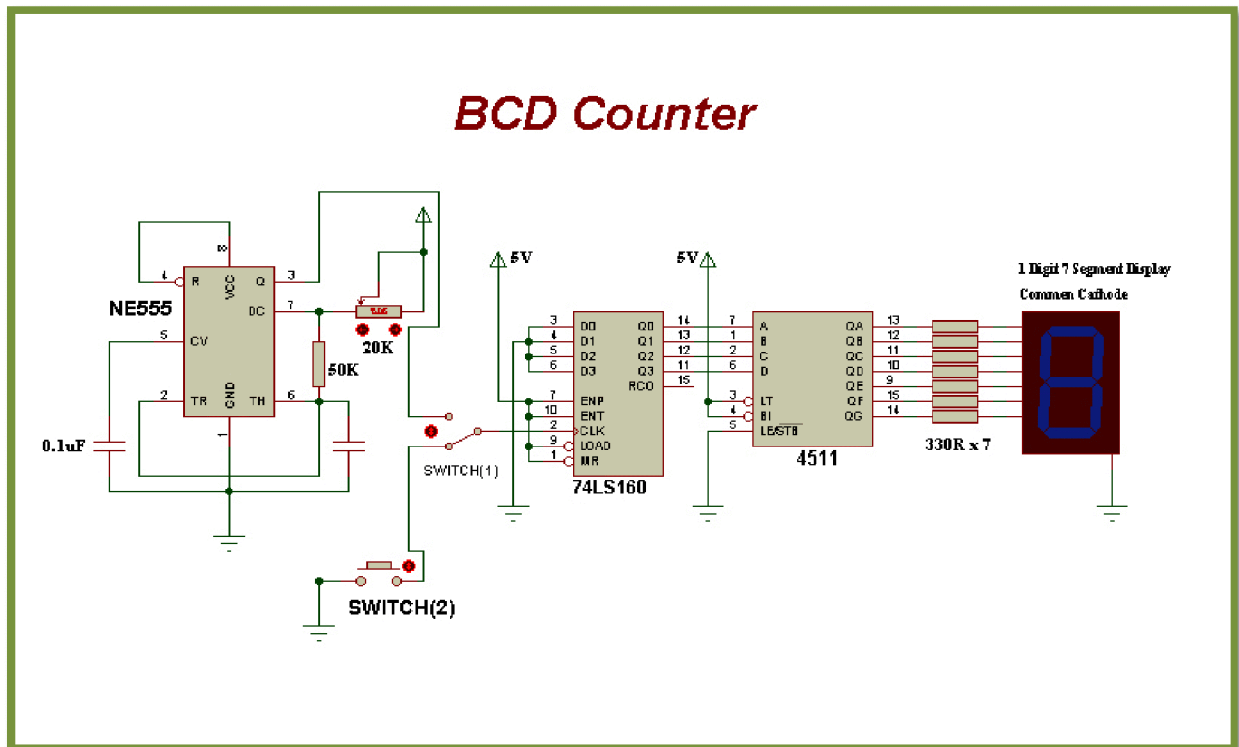


## BCD Counter Circuit



Circuit Diagram 01

BCD Counter circuit use for count up to 0-9. NE555 timer use to make pulse to drive counter part of circuit, but you can add debounce less switch (Circuit Diagram 02) without timer.

### Parts List for Circuit Diagram 01

Common Cathode 7 Segment (01)

NE555 (01)

74LS160 (01)

4511 (01)

330R (07)


20K Preset (01)

50K (01)

0.1uF (01)


10uF (01)

### For real world simulation

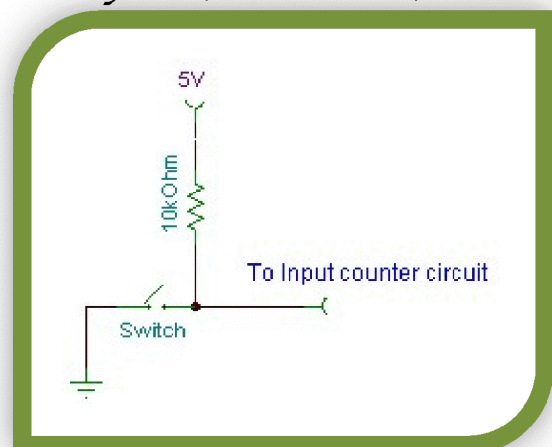

Circuit Diagram 02

## BCD Counter Circuit 2

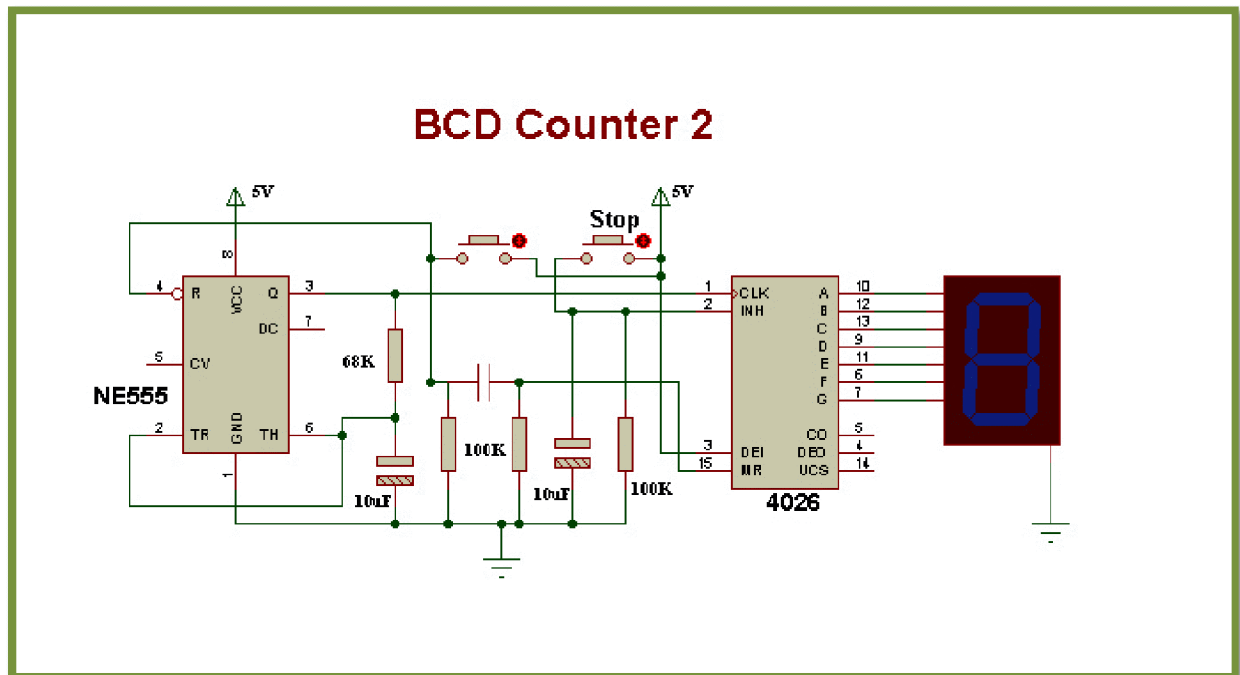

*Circuit Diagram 03*

*This circuit diagram result is same as above circuit and you can add debounce less switch too.*

*Pars list for Circuit Diagram 03*

*Common Cathode 7 Segment (01)*

*NE555 (01)*

*4026 (01)*

*100K (01)*

*68K (01)*

*10uF (01)*

*1nF (01)*